

# Unit 04 Fundamental of Digital Circuits

## Half Adder and Full Adder

### ICT A/L 2020



**SAMANTHA RAJAPAKSHA**

M.Sc. in IT (SLIIT) B.Sc.(Engineering) University of Moratuwa

Contact: 0710826165

[www.64bits.lk](http://www.64bits.lk)

# Half Adder

- A half adder is used to add two binary digits together, A and B.
- It produces S, the sum of A and B, and the corresponding carry out C.
- Although by itself, a half adder is not extremely useful, it can be used as a building block for larger adding circuits (Full Adder).

<b>X</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>
<b>+ Y</b>	<b>+ 0</b>	<b>+ 1</b>	<b>+ 0</b>	<b>+ 1</b>
<b>C S</b>	<b>0 0</b>	<b>0 1</b>	<b>0 1</b>	<b>1 0</b>

<b>X</b>	<b>Y</b>	<b>C</b>	<b>S</b>
<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>1</b>	<b>0</b>



# Half Adder

X	Y	C
0	0	0
0	1	0
1	0	0
1	1	1

$$C = X \cdot Y$$

X	Y	S
0	0	0
0	1	1
1	0	1
1	1	0
 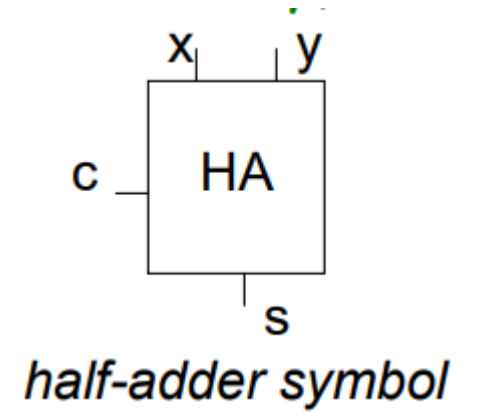
$$S = X \cdot \bar{Y} + \bar{X} \cdot Y = X \oplus Y$$



# Full Adder

- A full adder is similar to a half adder, but includes a carry-in bit from lower stages.
- Like the half adder, it computes a sum bit, S and a carry bit, C.

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Z	0	0	0	0
X	0	0	1	1
+ Y	+ 0	+ 1	+ 0	+ 1
<hr/>	<hr/>	<hr/>	<hr/>	<hr/>
C S	0 0	0 1	0 1	1 0


Z	1	1	1	1
X	0	0	1	1
+ Y	+ 0	+ 1	+ 0	+ 1
<hr/>	<hr/>	<hr/>	<hr/>	<hr/>
C S	0 1	1 0	1 0	1 1

# Full Adder

Full Adder Truth table

INPUTS			OUTPUTS	
A	B	C <sub>in</sub>	SUM	CARRY <sub>OUT</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$C_{out} = AB + A C_{in} + B C_{in}$$

 

$$C_{out} = \bar{A}.B.C_{in} + A.\bar{B}.C_{in} + A.B.\bar{C}_{in} + A.B.C_{in}$$


$$A \oplus B = A \cdot \bar{B} + \bar{A} \cdot B$$

# Full Adder

Full Adder Truth table


INPUTS			OUTPUTS	
A	B	C <sub>in</sub>	SUM	CARRY <sub>OUT</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**XOR (Exclusive-OR)**

 

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0


**XNOR (Exclusive-NOR)  
(Equivalence)**

 


x	y	XNOR
0	0	1
0	1	0
1	0	0
1	1	1

$$\begin{aligned}
 \text{Sum} &= \bar{A} \bar{B} C_{in} + \bar{A} B \bar{C}_{in} + A \bar{B} \bar{C}_{in} + A B C_{in} \\
 &= C_{in} (\bar{A} \bar{B} + AB) + \bar{C}_{in} (\bar{A} B + A \bar{B}) \\
 &= C_{in} (A \odot B) + \bar{C}_{in} (A \oplus B) \\
 &= C_{in} (\overline{A \oplus B}) + \bar{C}_{in} (A \oplus B) \\
 &= C_{in} \oplus (A \oplus B)
 \end{aligned}$$

# Full Adder using two half Adder

 
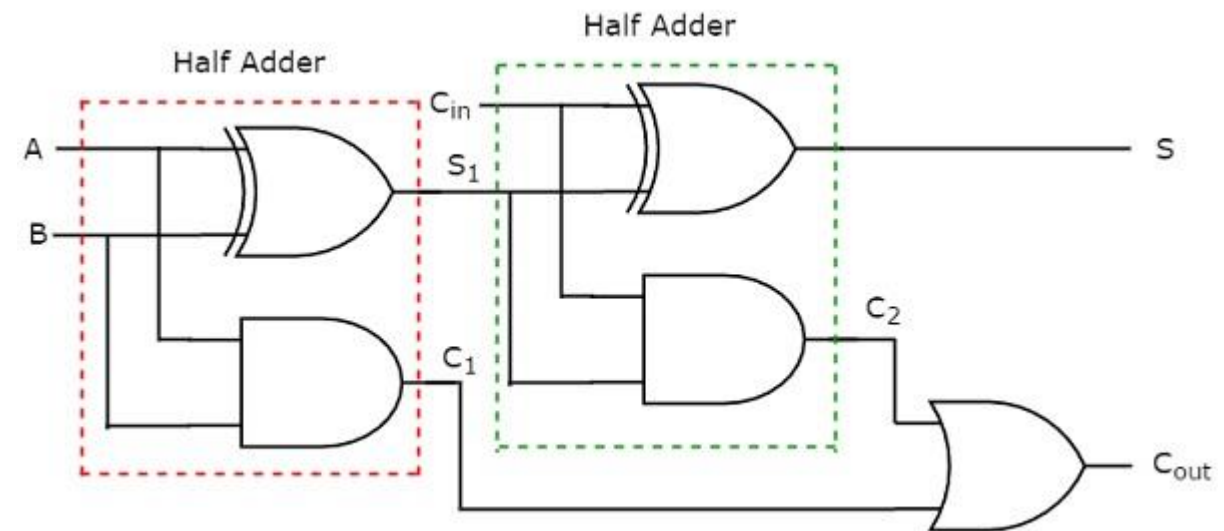
$$\begin{aligned}
 C_o &= \bar{A}BC_i + A\bar{B}C_i + AB\bar{C}_i + ABC_i \\
 &= C_i(\bar{A}B + A\bar{B}) + AB(\bar{C}_i + C_i) \\
 &= C_i(A \oplus B) + AB
 \end{aligned}$$



# Flip Flop

- **Combinational circuits:** Output depends only on the input of that time.
- **Sequential Circuit:** Output depends not only on the present inputs but also on the previous inputs and outputs.
- This type of circuit is required to perform sequence of actions without getting any further inputs. Use for memory storage (SRAM).
- Flip flops can also be considered as the most basic idea of a Random-Access Memory. When a certain input value is given to them, they will be remembered.




# SR Latch

Flip-flops is called a bi-stable device, since it has only two possible stable output states: 1 (high) and 0 (low).

It has the capability of remaining in a particular state until input signal cause it to change.

 - S is the SET input, R is RESET input
- Q and  $\bar{Q}$  are the complementary outputs



1. As long as the inputs  $S$  and  $R$  are both 0, the outputs of the flip-flop remain unchanged.
2. When  $S$  is 1 and  $R$  is 0, the flip-flop is *set* to  $Q = 1$  and  $\bar{Q} = 0$ .
3. When  $S$  is 0 and  $R$  is 1, the flip-flop is *reset* to  $Q = 0$  and  $\bar{Q} = 1$ .
4. It is “not allowed” (NA) to place a 1 on  $S$  and  $R$  simultaneously since the output will be unpredictable.


# SR Latch

A flip-flop circuit can be constructed from two NAND gates or two NOR gates.

Flip-flop has two outputs, Q and  $Q'$ , and two inputs, set and reset.


This type of flip-flop is referred to as an SR flip-flop or SR latch.
 
## Basic flip-flop circuit with NOR gates



# SR Latch

 
## Basic flip-flop circuit with NAND gates (NAND latch)




S	R	Q	$\bar{Q}$	
1	0	0	1	
1	1	0	1	(after S=1, R=0)
0	1	1	0	
1	1	1	0	(after S=0, R=1)
0	0	1	1	← NA
 
# SR Latch Using NAND gates

NAND latch has two possible resting states when SET = CLEAR = 1.




After S=1, R=0

 


After S=0, R=1


**Figure** Pulsing the SET input to the 0 state will always produce the  $Q = 1, \bar{Q} = 0$ :  
 output state (a)  $Q = 0$  prior to SET pulse; (b)  $Q = 1$  prior to SET pulse.

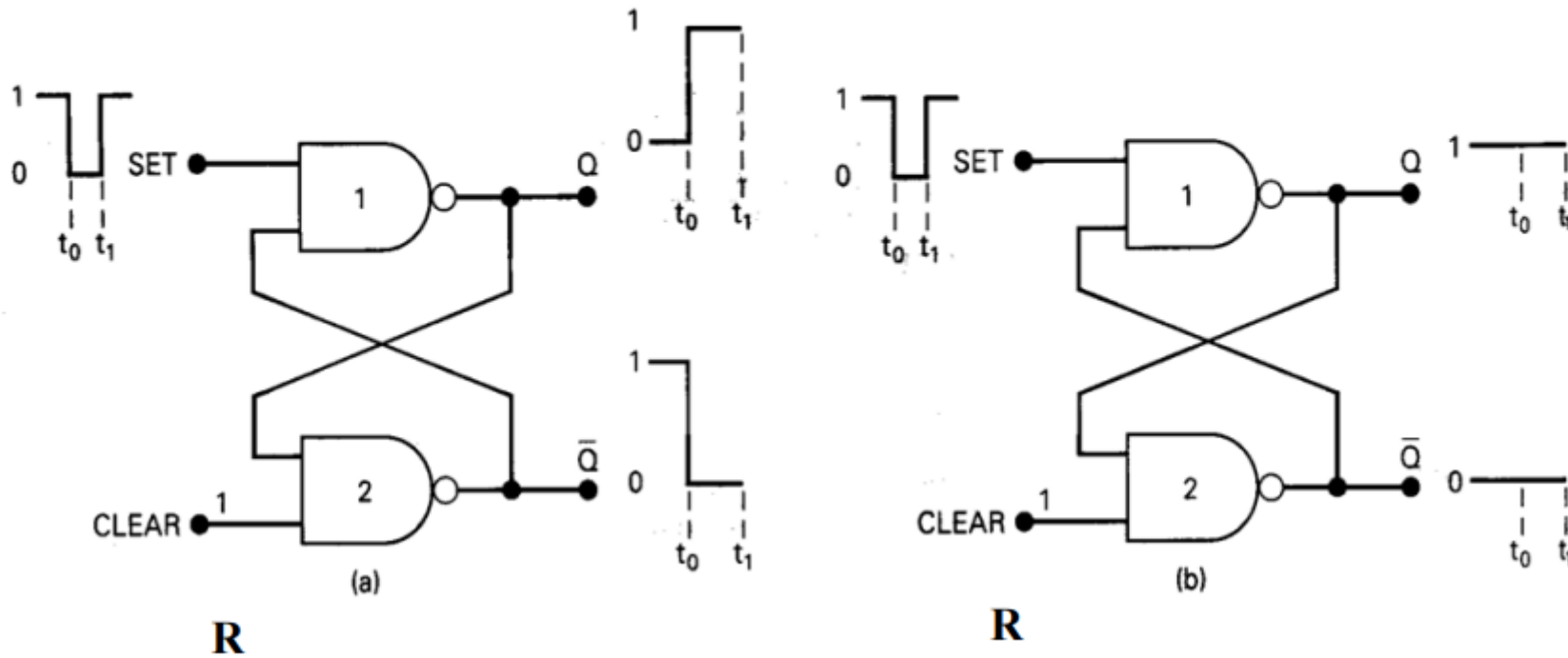

**Figure** Pulsing the CLEAR input to the LOW state will always produce  $Q = 0, \bar{Q} = 1$ :

 (a)  $Q = 0$  prior to CLEAR pulse; (b)  $Q = 1$  prior to CLEAR pulse.



 

Set	Clear	Output
1	1	No change
0	1	$Q = 1$
1	0	$Q = 0$
0	0	Invalid*

\*produces  $Q = \bar{Q} = 1$

(b)

(a) NAND latch; (b) truth table.